
	HACETTEPE UNIVERSITY ELECTRICAL AND ELECTRONICS ENGINEERING ELE227 PRELIMINARY WORK #1
Name	Muhammed Baki Almacı
Student ID	21627983

1) Convert following decimal numbers to 8-bit binary numbers

2) Convert following 8-bit binary numbers to decimal and hexadecimal

3)

a.

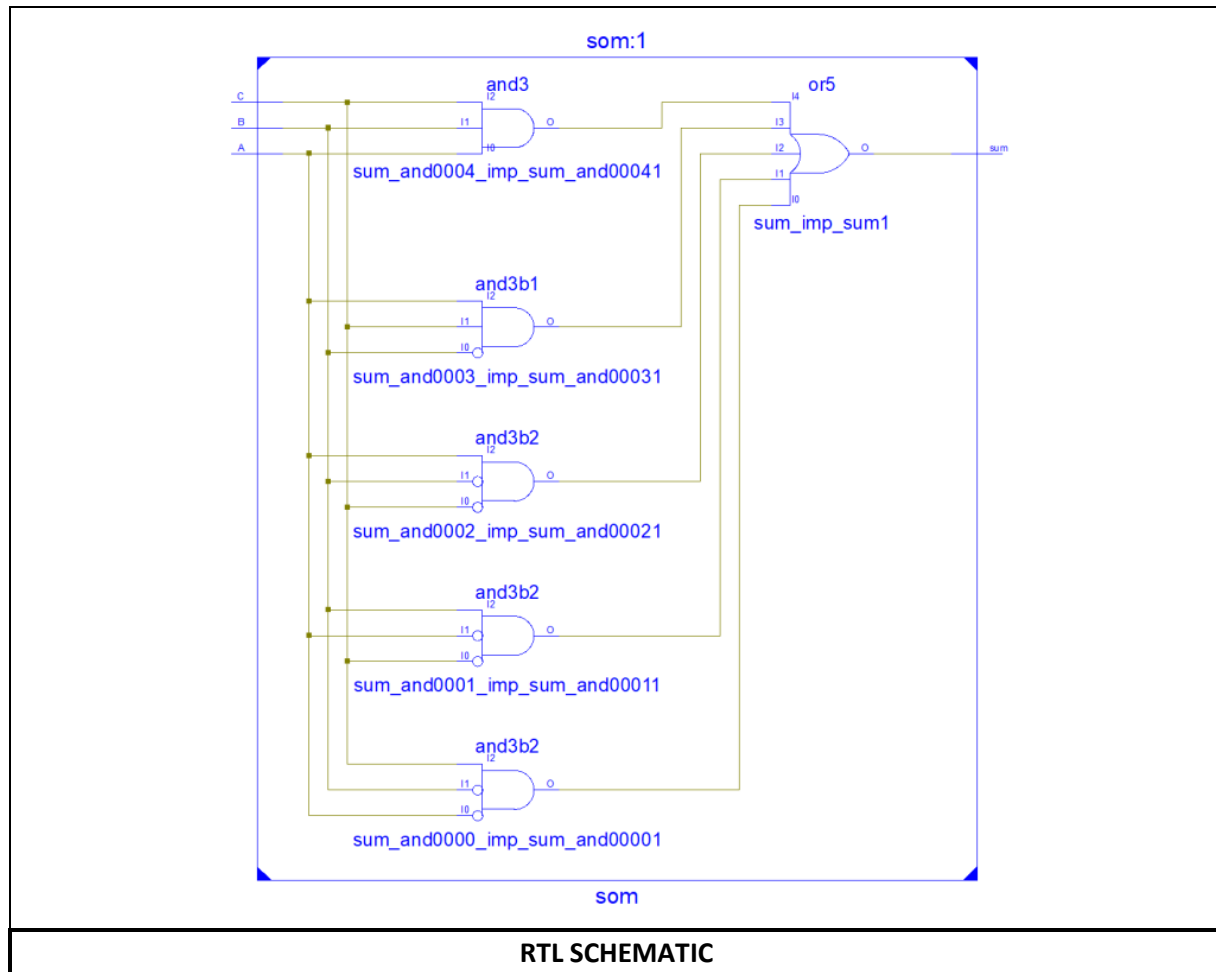

RTL SCHEMATIC

```

library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

entity som is
  Port ( A : in STD_LOGIC;
        B : in STD_LOGIC;
        C : in STD_LOGIC;
        sum : out STD_LOGIC);
end som;

architecture Behavioral of som is

begin
  sum <= ((NOT A) AND (NOT B) AND C) OR ((NOT A) AND (B) AND (NOT C)) OR ((A) AND
(NOT B) AND (NOT C)) OR ((A) AND (NOT B) AND C) OR((A) AND (B) AND (C));


end Behavioral;

```

VHDL CODE

b.

<pre> stim_proc: process begin A <= '0'; B <= '0'; C <= '0'; wait for 100 ns; A <= '0'; B <= '0'; C <= '1'; wait for 100 ns; A <= '0'; B <= '1'; C <= '0'; wait for 100 ns; A <= '0'; B <= '1'; C <= '1'; wait for 100 ns; </pre>	<pre> A <= '1'; B <= '0'; C <= '0'; wait for 100 ns; A <= '1'; B <= '0'; C <= '1'; wait for 100 ns; A <= '1'; B <= '1'; C <= '0'; wait for 100 ns; A <= '1'; B <= '1'; C <= '1'; wait; end process; </pre>
TEST BENCH CODE	

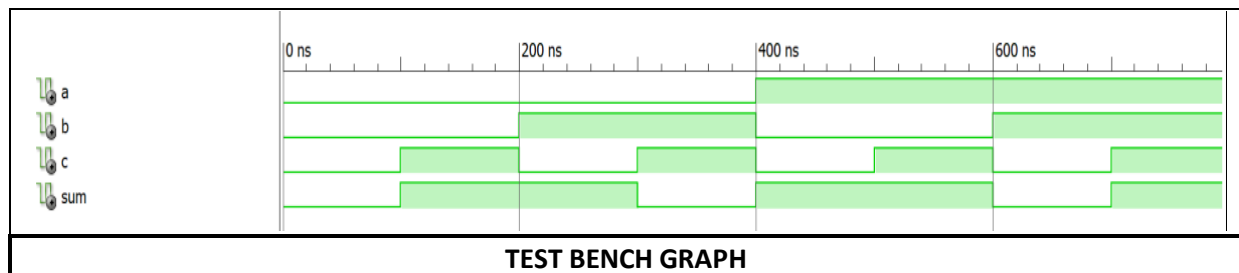

TEST BENCH GRAPH


4)

a.

b.

c.

d.

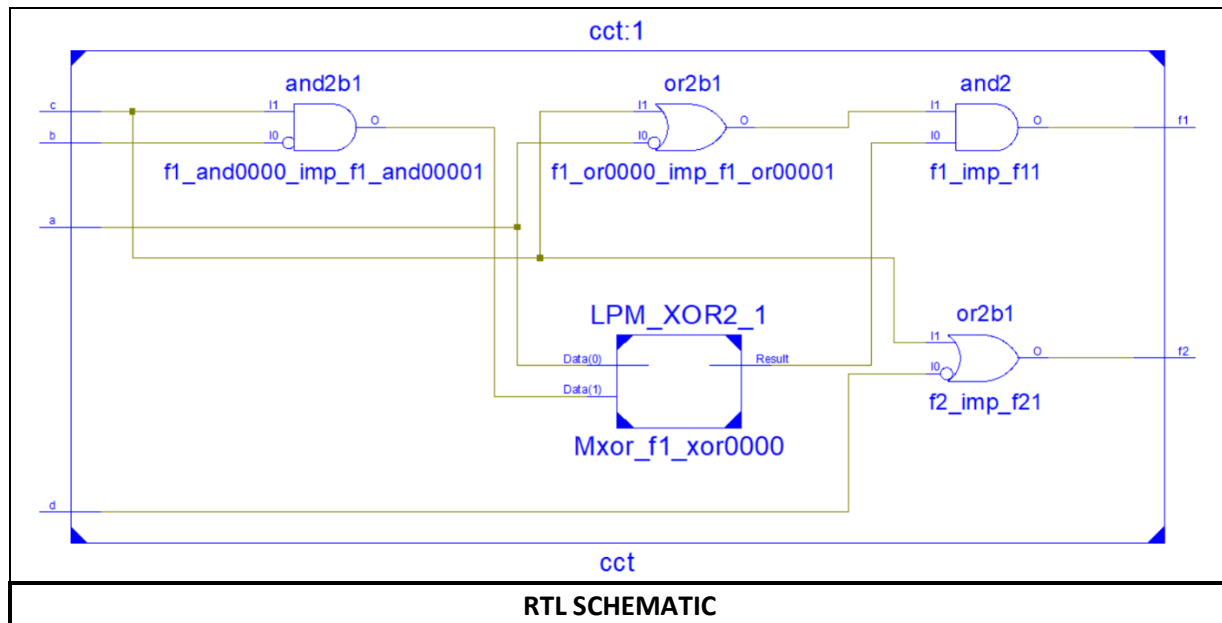

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
```

```
entity cct is
```

```
  Port ( a : in STD_LOGIC;
        b : in STD_LOGIC;
        c : in STD_LOGIC;
        d : in STD_LOGIC;
        f1 : out STD_LOGIC;
        f2 : out STD_LOGIC);
```

```
end cct;
```

```
architecture Behavioral of cct is
```

```
begin
```

```
  f1 <= ((c and (not b)) xor a) and ((not a) or c);
```


```
  f2 <= (c and d) or (not d);
```

```
end Behavioral;
```

VHDL CODE

e.

<pre> stim_proc: process begin -- hold reset state for 100 ns. a <= '0'; b <= '0'; c <= '0'; d <= '0'; wait for 100 ns; a <= '0'; b <= '0'; c <= '0'; d <= '1'; wait for 100 ns; a <= '0'; b <= '1'; c <= '1'; d <= '0'; wait for 100 ns; </pre>	<pre> a <= '1'; b <= '1'; c <= '1'; d <= '1'; wait for 100 ns; wait; end process; </pre>
TEST BENCH CODE	

 


5)

a.

b.

c.

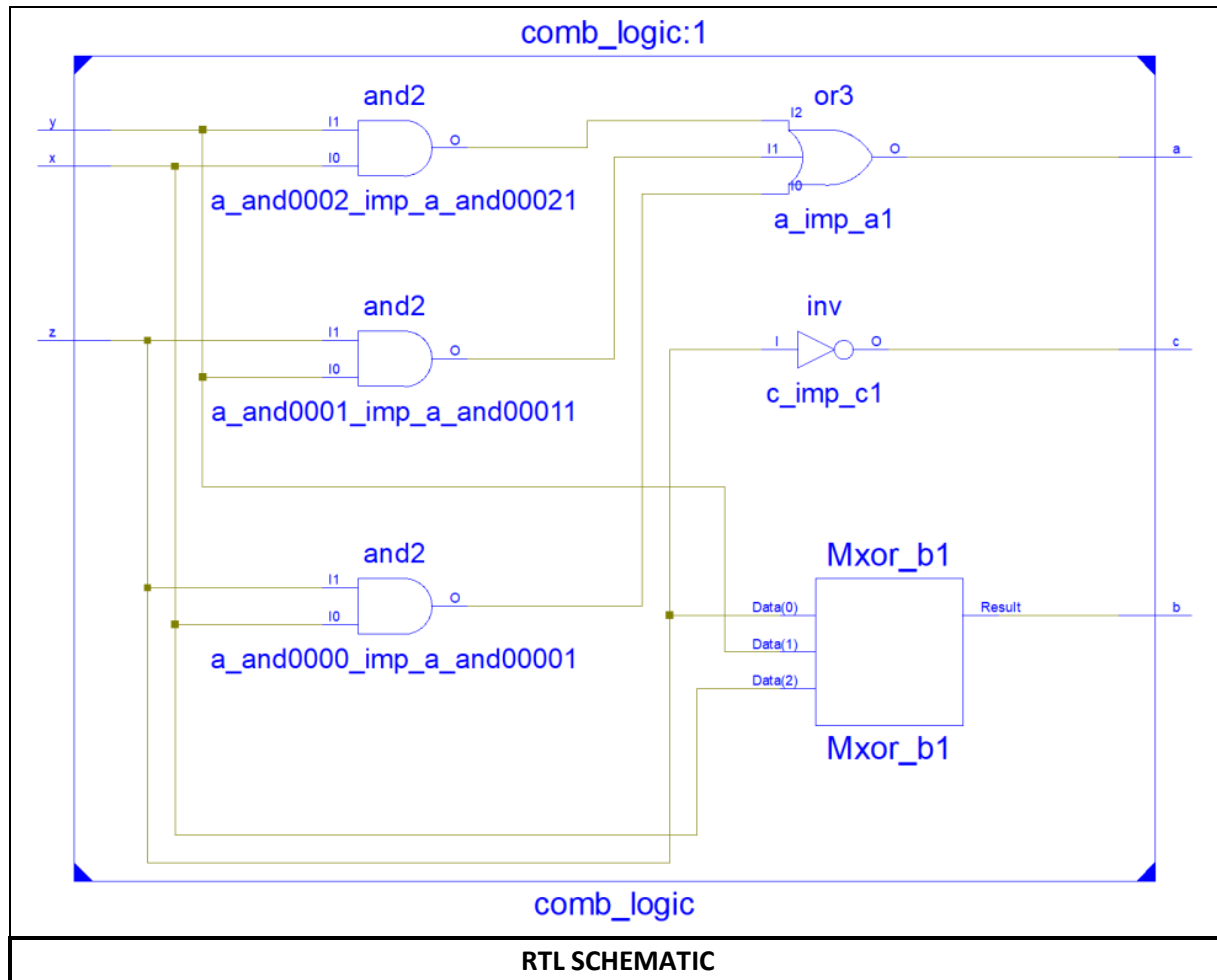

```

library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

entity comb_logic is
  Port ( x : in  STD_LOGIC;
        y : in  STD_LOGIC;
        z : in  STD_LOGIC;
        a : out STD_LOGIC;
        b : out STD_LOGIC;
        c : out STD_LOGIC);
end comb_logic;

architecture Behavioral of comb_logic is

begin
  a <= (x and z) or (y and z) or (x and y);
  b <= x xor y xor z;
  c <= not z;


end Behavioral;

```

VHDL CODE

d.

<pre> stim_proc: process begin x <= '0'; y <= '0'; z <= '0'; wait for 100 ns; x <= '0'; y <= '0'; z <= '1'; wait for 100 ns; x <= '0'; y <= '1'; z <= '0'; wait for 100 ns; x <= '0'; y <= '1'; z <= '1'; wait for 100 ns; </pre>	<pre> x <= '1'; y <= '0'; z <= '0'; wait for 100 ns; x <= '1'; y <= '0'; z <= '1'; wait for 100 ns; x <= '1'; y <= '1'; z <= '0'; wait for 100 ns; x <= '1'; y <= '1'; z <= '1'; wait; end process; </pre>
TEST BENCH CODE	

 

TEST BENCH GRAPH