



Quiz 3:

Q) There is a digital device, that contains a combinational logic circuit. This system has 3 binary inputs (x, y, z) and 3 binary outputs (A, B, C). An electrical and electronics engineering student (like you) observes this system by applying all possible inputs and recording all possible outputs. After some observation of the behavior of the system, student has reached following results:

- With all these given information,

- [illegible]